
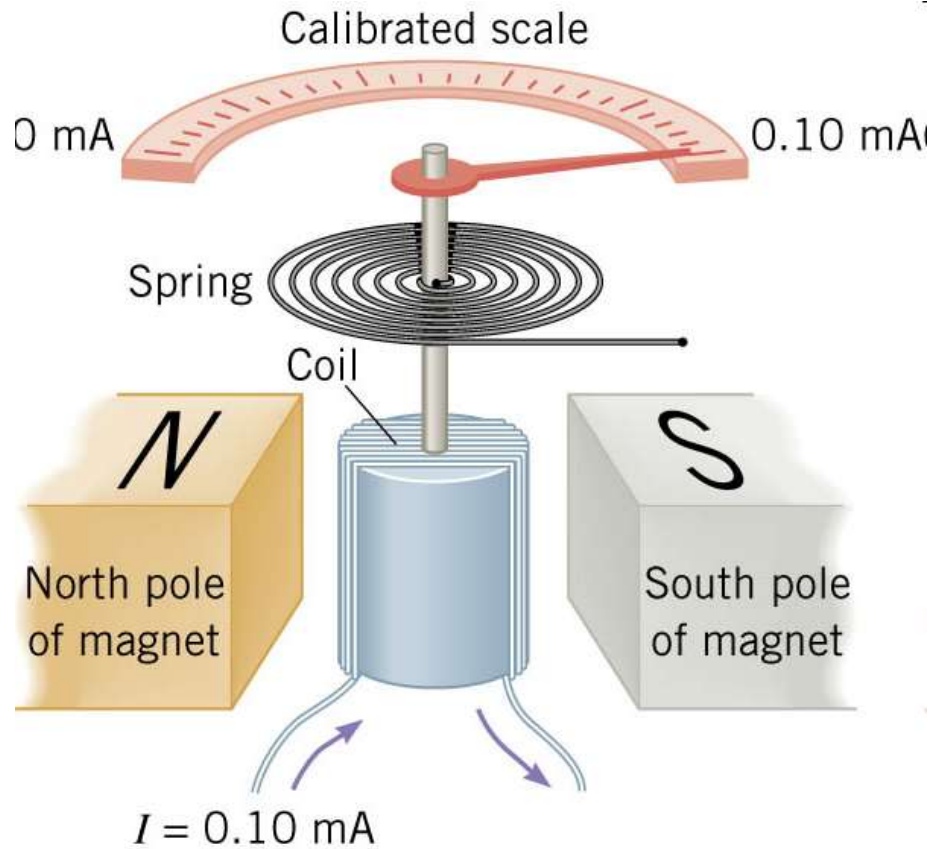


Ammeters & Voltmeters

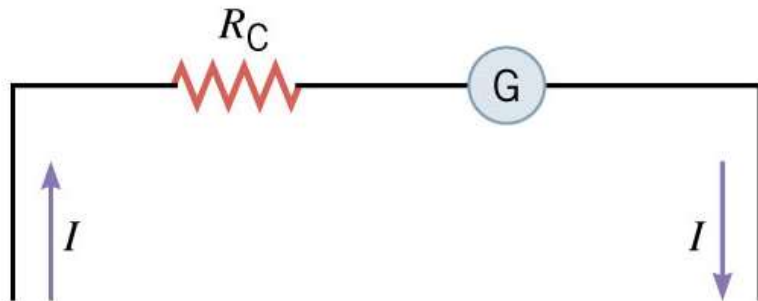

(a)




A coil of wire in a magnetic field twists proportionally to the current.

Galvanometer.

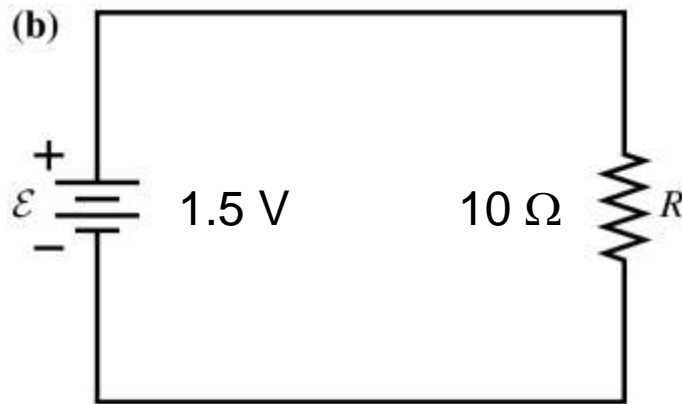
Problem – resistance R_C wrong size to use alone to measure I or V .

The Problem – Galvanometer not a good Ammeter


- We want to measure I for a circuit where either V or R is unknown.
- But if R_C is big compared to R , I is wrong



$$I = V/R = 1.5 / 10 = 0.15 \text{ A}$$

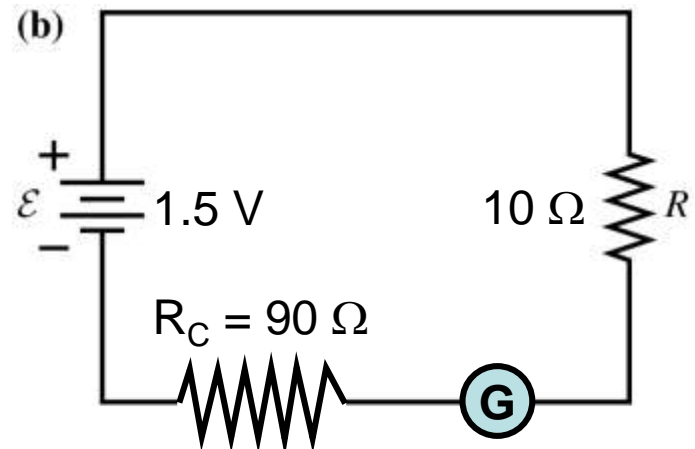
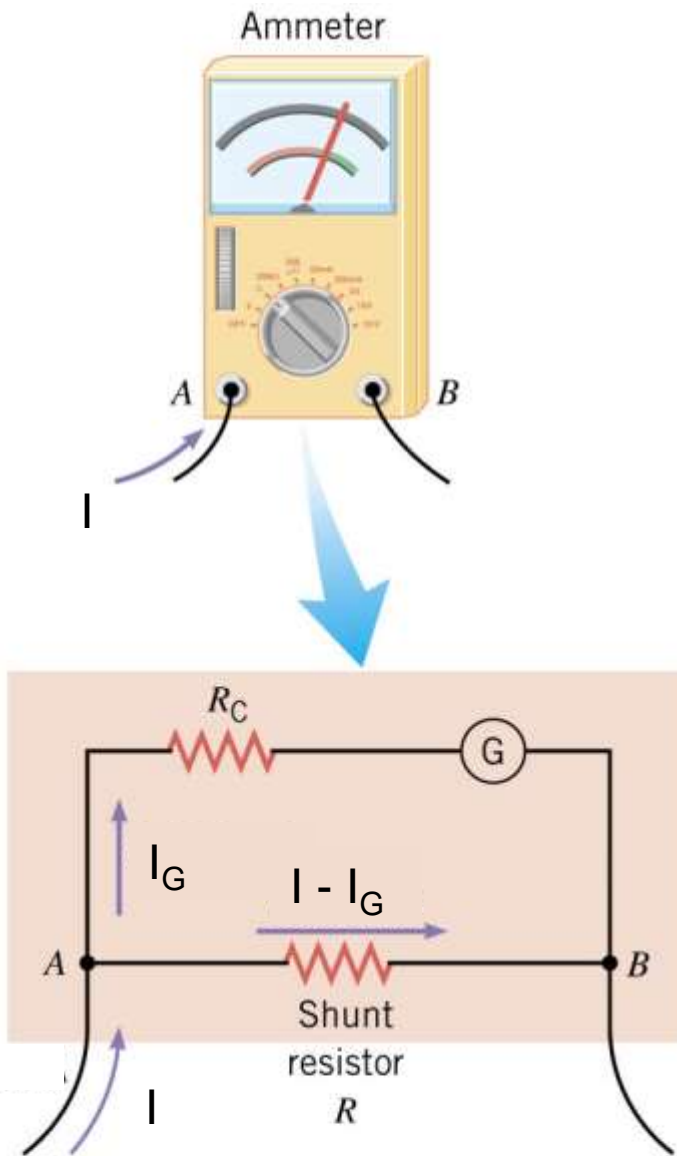
$$I = V/R_{EQ} = 1.5 / 100 = 0.015 \text{ A}$$



Ammeter

We construct an ammeter by connecting a small shunt resistor in parallel.


Shunt carries most of the current.

$$I_G R_C = (I - I_G) R_{shunt}$$

$$\frac{1}{R_A} = \frac{1}{R_C} + \frac{1}{R_{shunt}}$$


The Problem – Galvanometer not a good Voltmeter

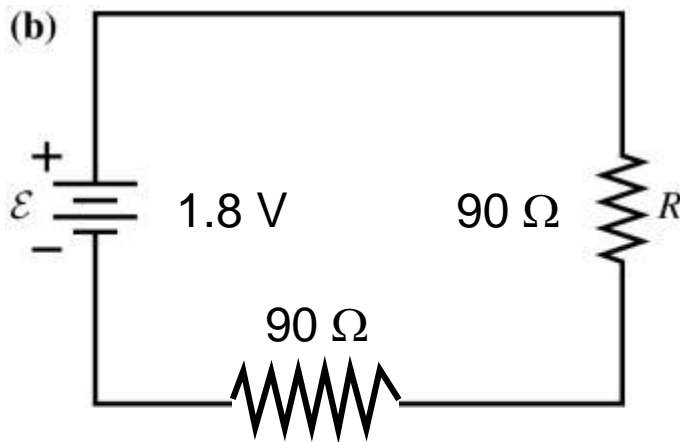- But if R_C is not big compared to R , V is wrong



$$I = V_B / (R+90) = 0.01 \text{ A}$$

$$V_R = 90 \times 0.01 = 0.9 \text{ V}$$

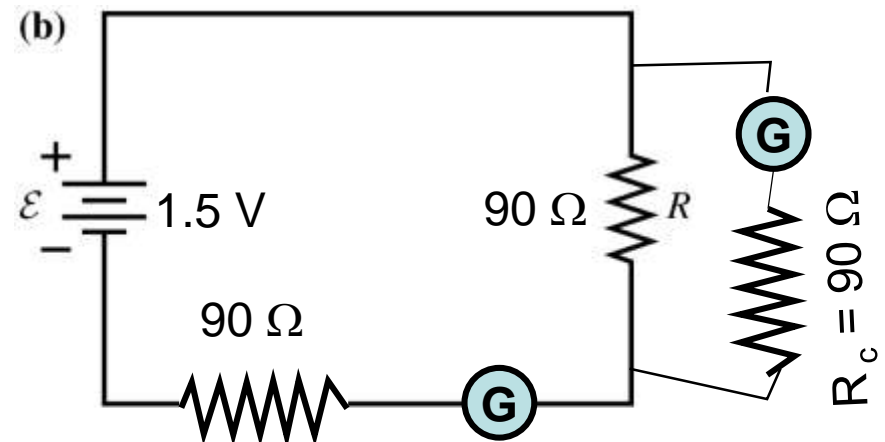

$$R_{EQ} = 90 + (1/90 + 1/90)^{-1} = 135 \Omega$$

$$I = 1.8 / 135 = 0.013333 \text{ A}$$

$$V_G = I_G R_C = (0.013333/2)90 = 0.6 \text{ V}$$


Voltmeter

We construct a voltmeter by connecting a large multiplier resistor in series.

Need $R_M + R_c \gg R$ by about 100 times

$$V = (R_{\text{multiplier}} + R_c) I_G$$

$$R_V = R_{\text{multiplier}} + R_c$$

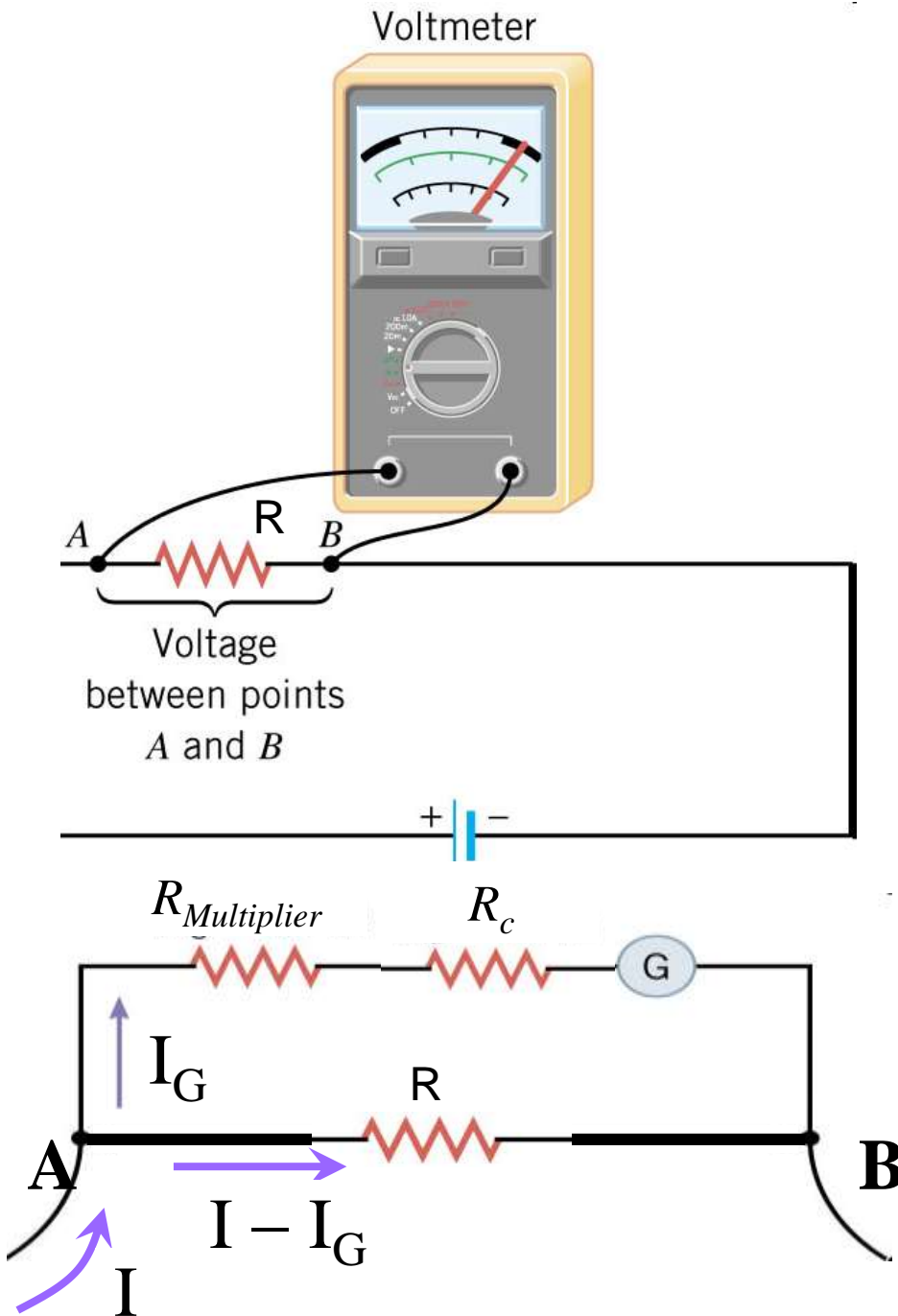

Remember

- Ammeters have a small resistance, make sure $R_A \ll R$
- Connect in series
- Voltmeters have a large resistance, make sure $R_V \gg R$
- Connect in parallel